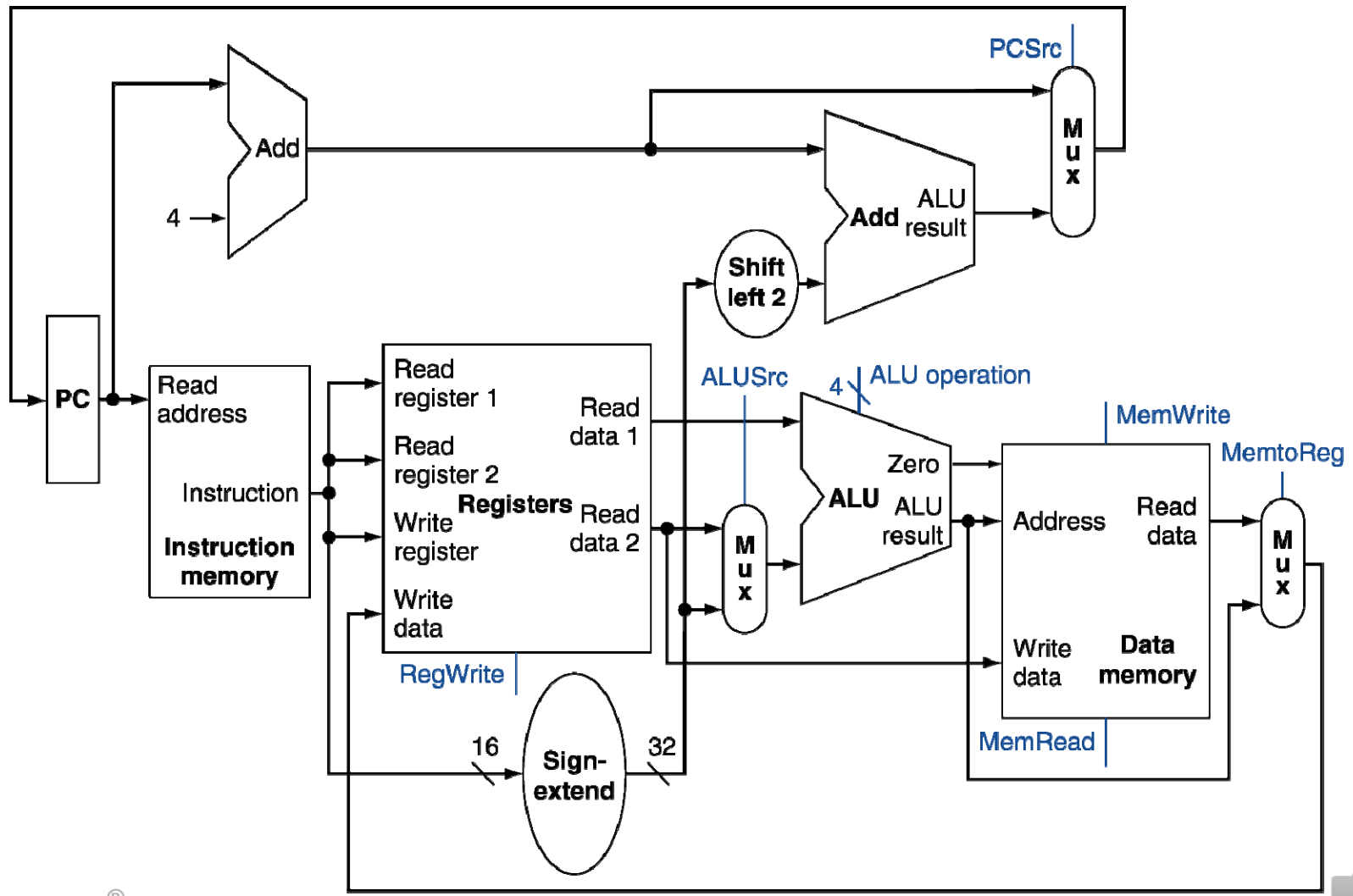


# Chapter 4

## The Processor



# Full Datapath



# ALU Control

- ALU used for
  - Load/Store: F = add
  - Branch: F = subtract
  - R-type: F depends on funct field

ALU control	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set-on-less-than
1100	NOR



# ALU Control


- Assume 2-bit ALUOp derived from opcode
  - Combinational logic derives ALU control

opcode	ALUOp	Operation	funct	ALU function	ALU control
lw	00	load word	XXXXXX	add	0010
sw	00	store word	XXXXXX	add	0010
beq	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
		subtract	100010	subtract	0110
		AND	100100	AND	0000
		OR	100101	OR	0001
		set-on-less-than	101010	set-on-less-than	0111



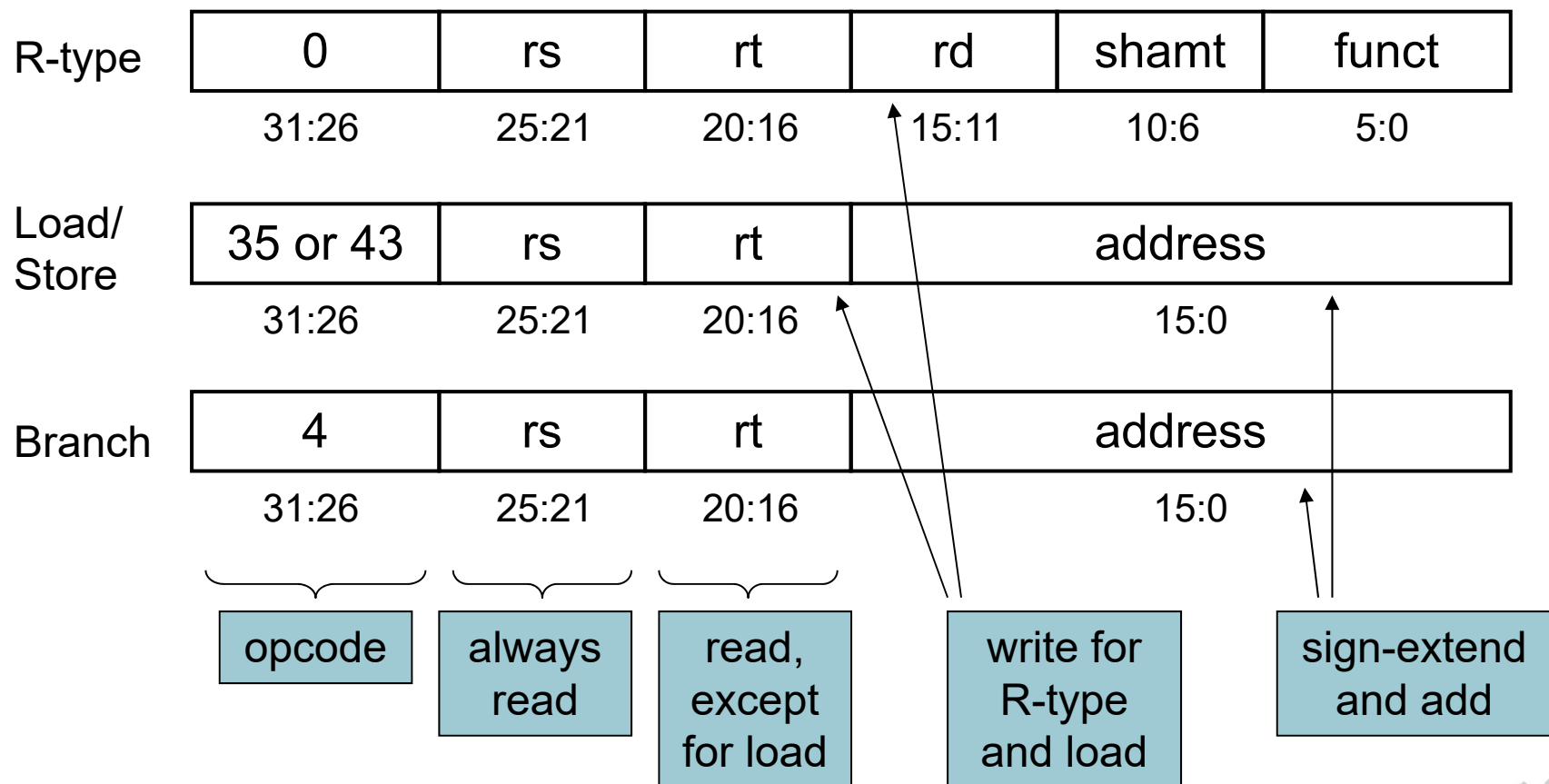
# The Main Control Unit


- Control signals derived from instruction




# Datapath With Control

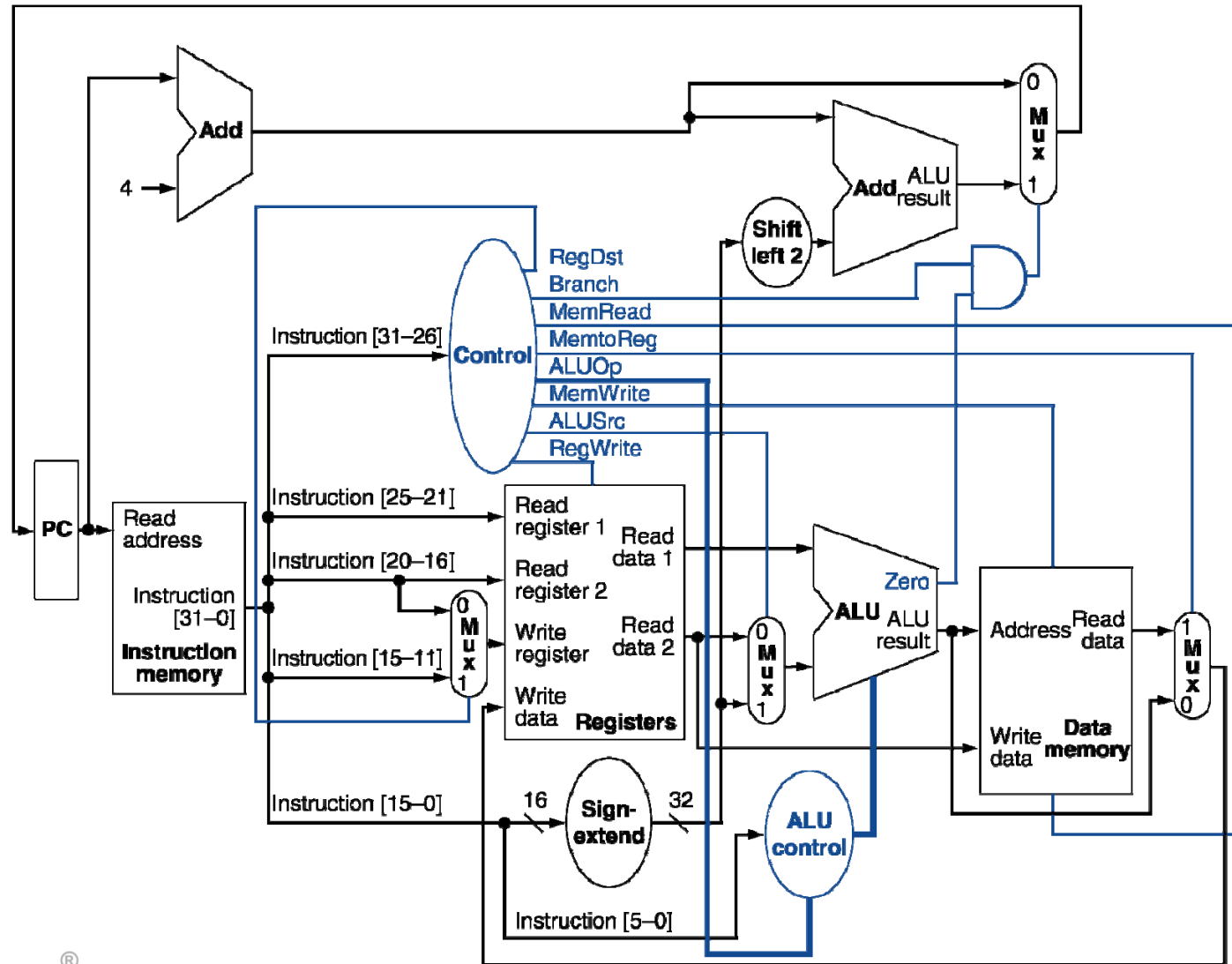

# R-Type Instruction

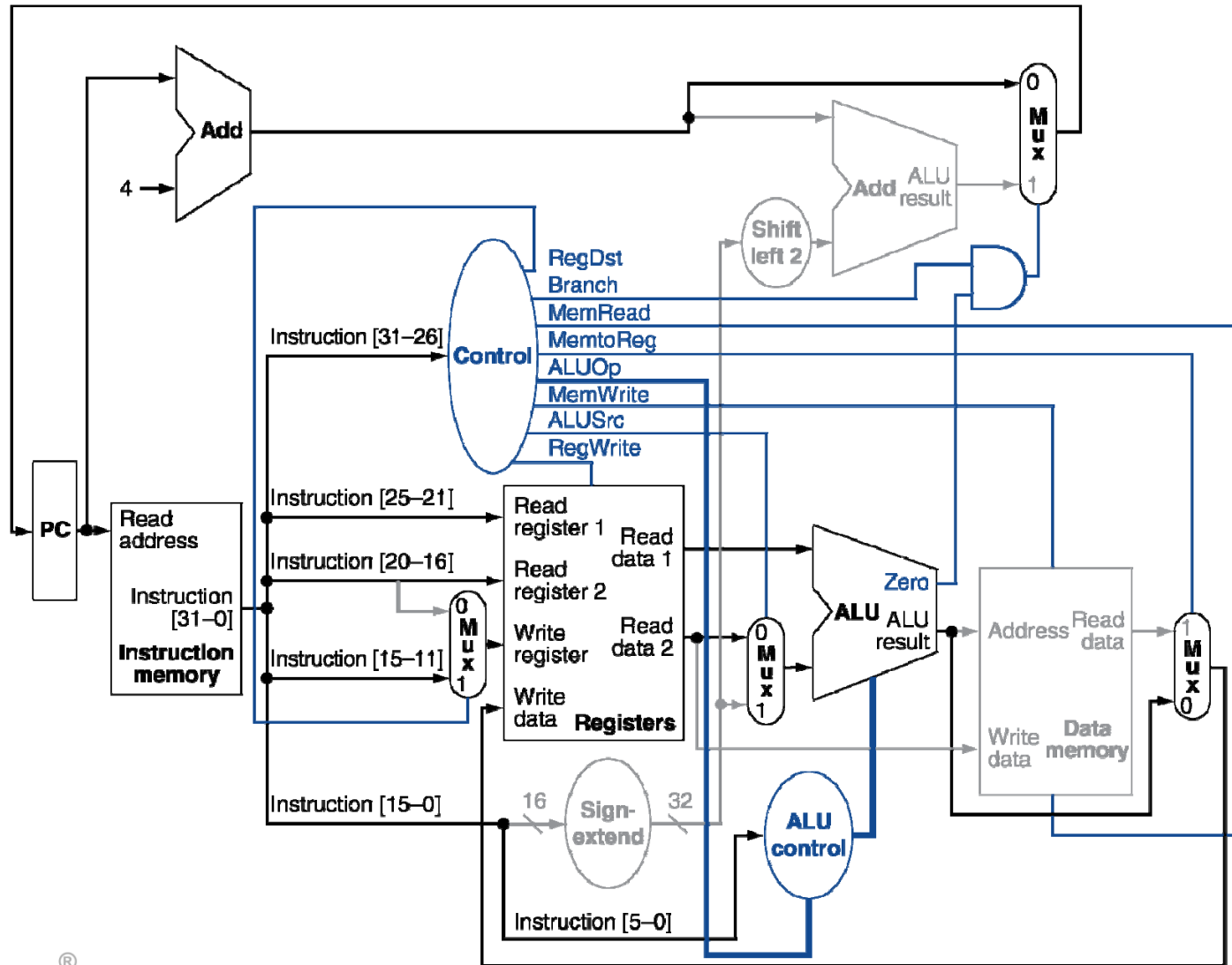


# Load Instruction

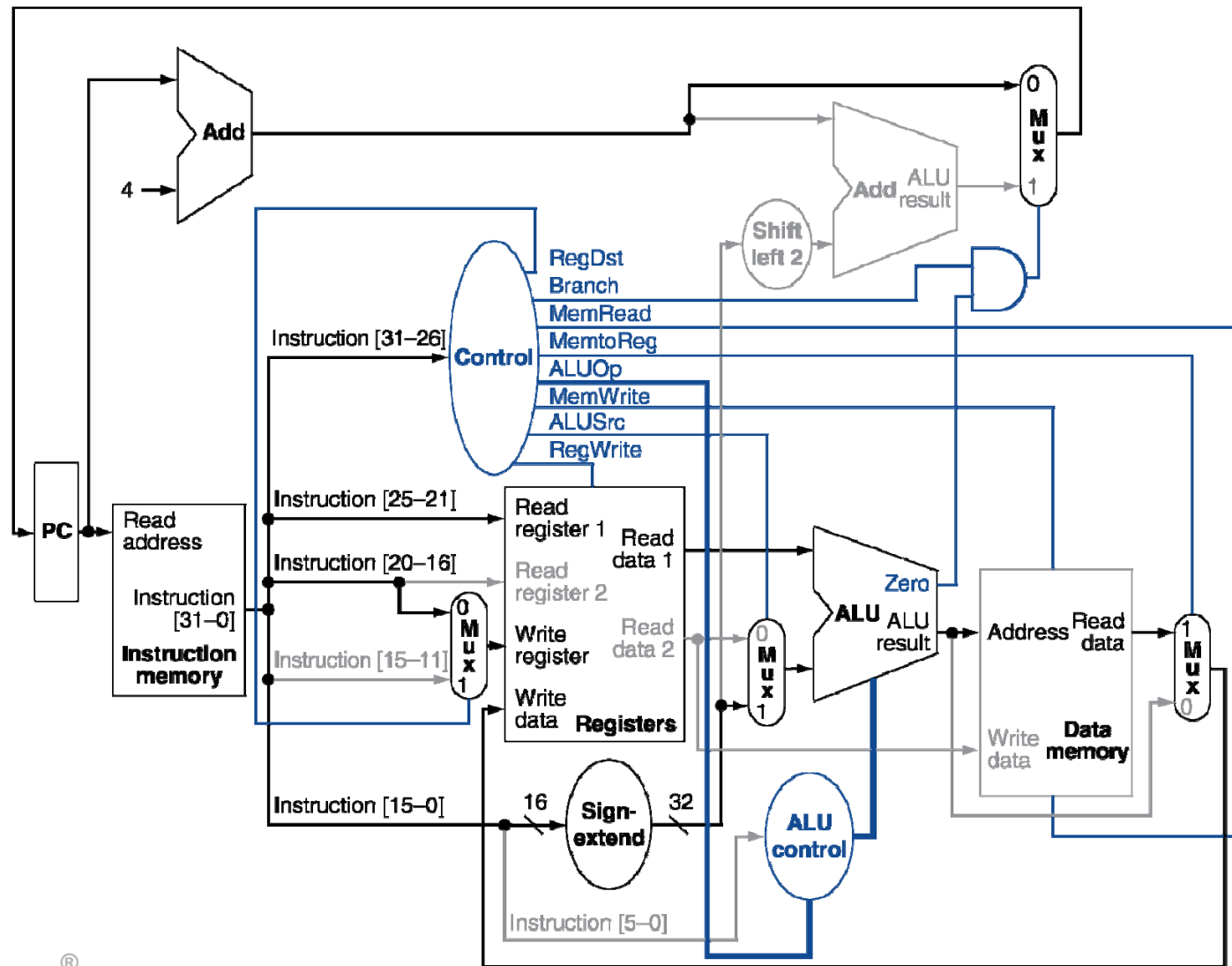




# Branch-on-Equal Instruction

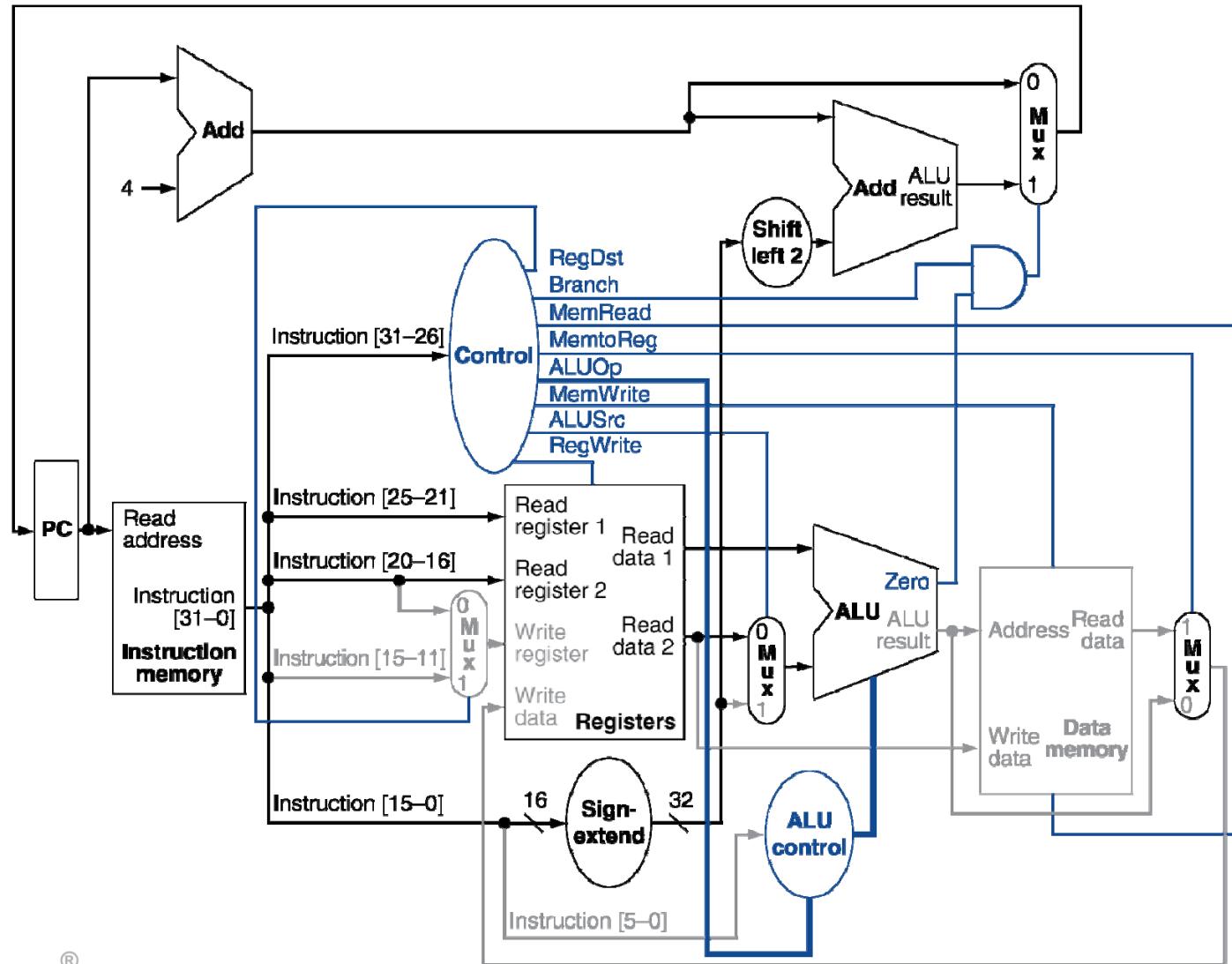


# Controller

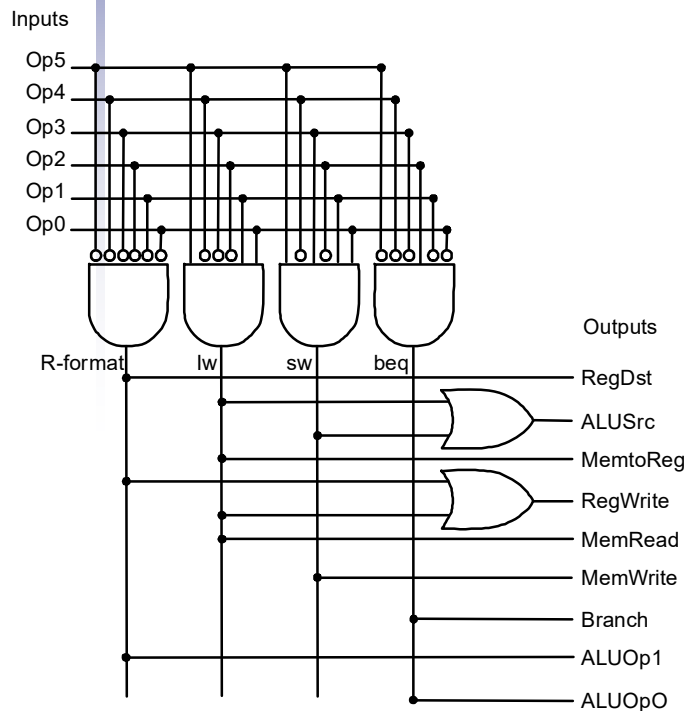

		R-format	lw	sw	beq
Opcode		000000	100011	101011	000100
Outputs	RegDst	1	0	X	X
	ALUSrc	0	1	1	0
	MemtoReg	0	1	X	X
	RegWrite	1	1	0	0
	MemRead	0	1	0	0
	MemWrite	0	0	1	0
	Branch	0	0	0	1
	ALUOp1	1	0	0	0
	ALUOp2	0	0	0	1




# Implementing Jumps

 

- Jump uses word address
- Update PC with concatenation of
  - Top 4 bits of old PC
  - 26-bit jump address
  - 00
- Need an extra control signal decoded from opcode



# Datapath With Jumps Added

 

# Up Next

- Pipelined Implementation
- Why isn't single cycle enough?
  - control is relatively simple
  - CPI is 1, but cycle time must be long enough for every instruction to complete!
  - branch instruction versus load instruction
    - loads require instruction fetch, register access, ALU, memory access, register access
    - branches require instruction fetch, register access, ALU
  - and this is for a simplified processor!
    - no floating point ops, no multiply or divide

