

# Chapter 3

## Arithmetic for Computers



# Arithmetic for Computers

- Operations on integers
  - Addition and subtraction
  - Multiplication and division
  - Dealing with overflow
- Floating-point real numbers
  - Representation and operations





# Integer Subtraction

- Add negation of second operand

- Example:  $7 - 6 = 7 + (-6)$

+7:	0000 0000 ... 0000 0111
-6:	1111 1111 ... 1111 1010
<hr/>	
+1:	0000 0000 ... 0000 0001

- Overflow if result out of range

- Subtracting two +ve or two -ve operands, no overflow
- Subtracting +ve from -ve operand
  - Overflow if result sign is 0
- Subtracting -ve from +ve operand
  - Overflow if result sign is 1




# Dealing with Overflow

- Some languages (e.g., C) ignore overflow
  - Use MIPS addu, addui, subu instructions
- Other languages (e.g., Ada, Fortran) require raising an exception
  - Use MIPS add, addi, sub instructions
  - On overflow, invoke exception handler
    - Save PC in exception program counter (EPC) register
    - Jump to predefined handler address
    - mfc0 (move from coprocessor reg) instruction can retrieve EPC value, to return after corrective action




# Arithmetic Logic Unit Design

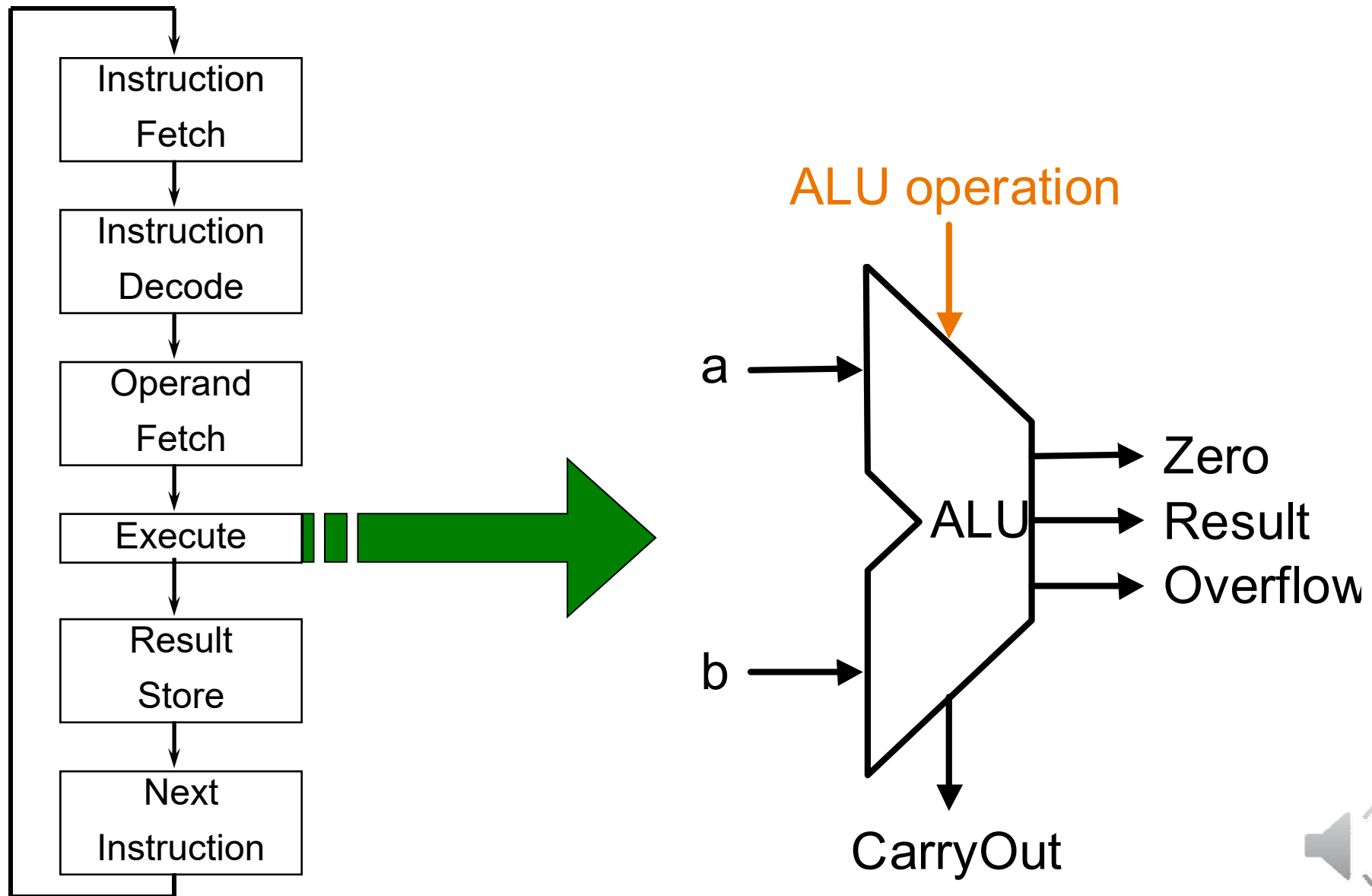

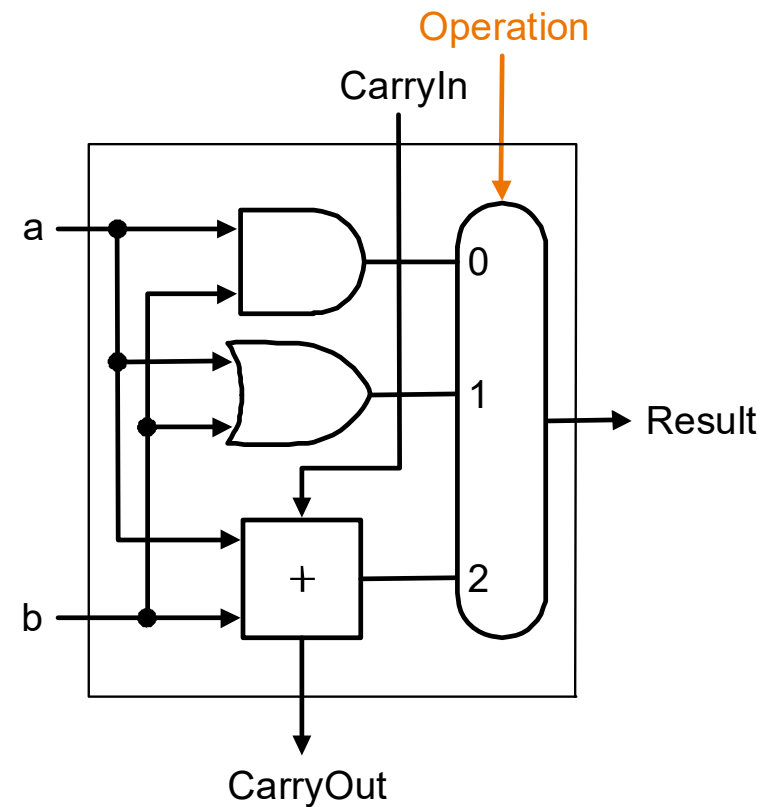
# One Bit ALU

- Performs AND, OR, and ADD
  - on 1-bit operands
  - components:
    - AND gate
    - OR gate
    - 1-bit adder
    - Multiplexor


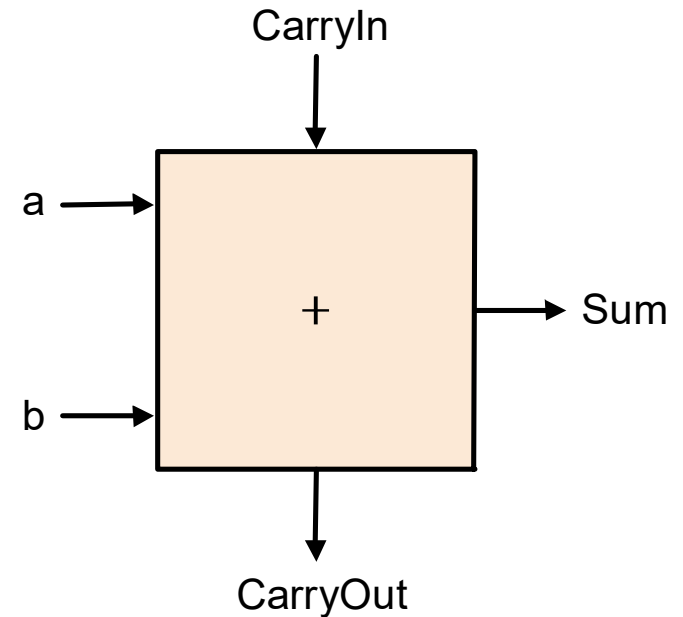
# One Bit Full Adder

- Also known as a (3,2) adder
- Half Adder
  - no CarryIn



Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	0+0+0=00
0	0	1	0	1	0+0+1=01
0	1	0	0	1	0+1+0=01
0	1	1	1	0	0+1+1=10
1	0	0	0	1	1+0+0=01
1	0	1	1	0	1+0+1=10
1	1	0	1	0	1+0+1=10
1	1	1	1	1	1+1+1=11





# CarryOut Logic Equation

- $\text{CarryOut} = (!a \ \& \ b \ \& \ \text{CarryIn}) \mid (a \ \& \ !b \ \& \ \text{CarryIn}) \mid (a \ \& \ b \ \& \ !\text{CarryIn}) \mid (a \ \& \ b \ \& \ \text{CarryIn})$
- $\text{CarryOut} = (b \ \& \ \text{CarryIn}) \mid (a \ \& \ \text{CarryIn}) \mid (a \ \& \ b)$

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	0+0+0=00
0	0	1	0	1	0+0+1=01
0	1	0	0	1	0+1+0=01
0	1	1	1	0	0+1+1=10
1	0	0	0	1	1+0+0=01
1	0	1	1	0	1+0+1=10
1	1	0	1	0	1+0+1=10
1	1	1	1	1	1+1+1=11



# Sum Logic Equation

- Sum =  $(!a \ \& \ !b \ \& \ \text{CarryIn}) \mid (!a \ \& \ b \ \& \ !\text{CarryIn}) \mid (a \ \& \ !b \ \& \ !\text{CarryIn}) \mid (a \ \& \ b \ \& \ \text{CarryIn})$

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	0+0+0=00
0	0	1	0	1	0+0+1=01
0	1	0	0	1	0+1+0=01
0	1	1	1	0	0+1+1=10
1	0	0	0	1	1+0+0=01
1	0	1	1	0	1+0+1=10
1	1	0	1	0	1+0+1=10
1	1	1	1	1	1+1+1=11

