


Chapter 3

Arithmetic for Computers




32-bit ALU

■ Ripple Carry ALU

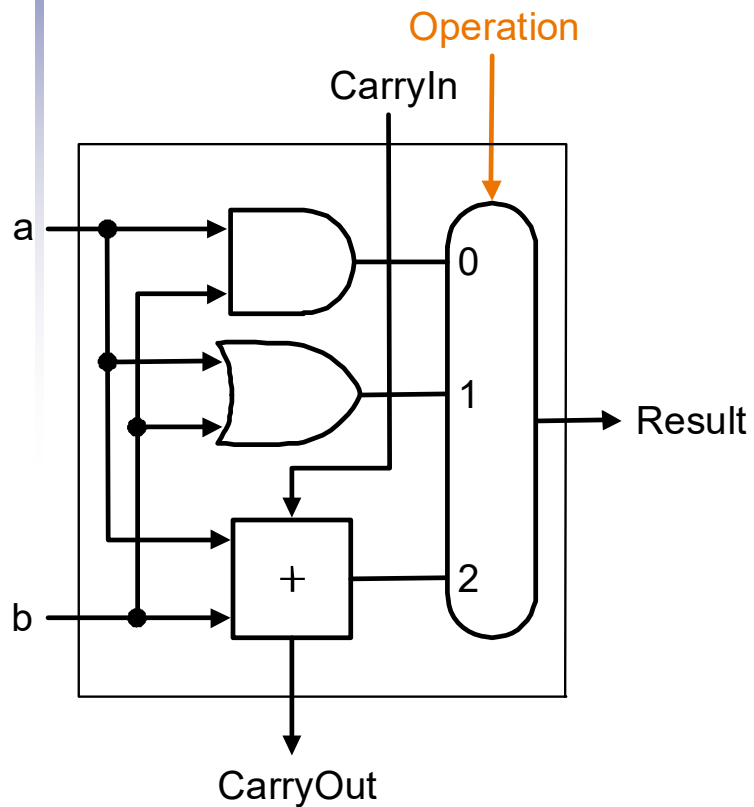

1-bit ALU

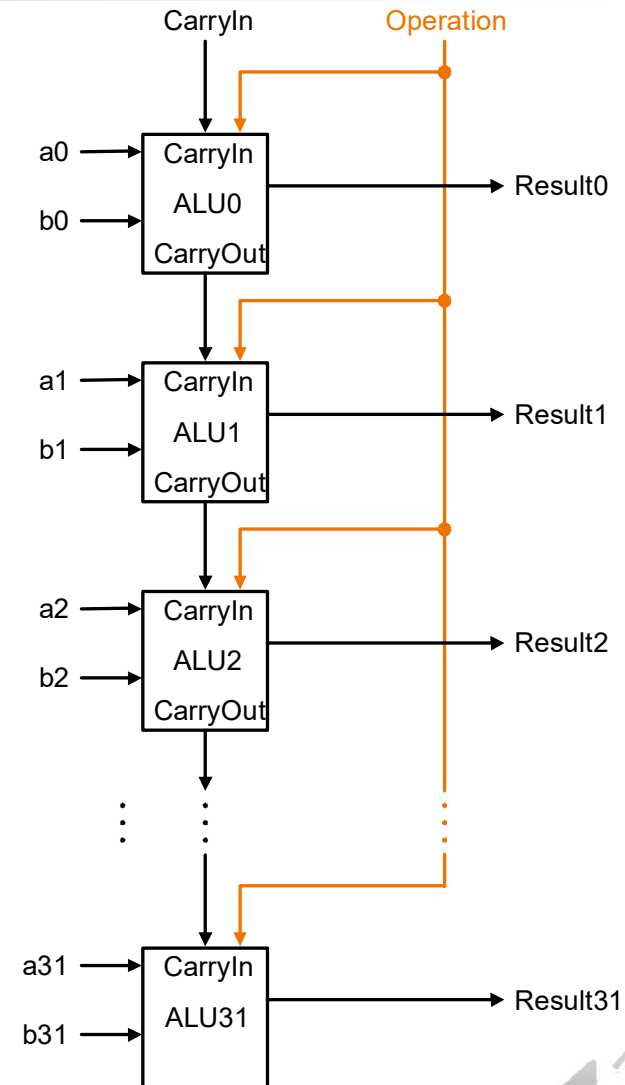


32-bit ALU



Subtraction?

 
- Expand our 1-bit ALU to include an inverter
 - 2's complement: take inverse of every bit and add 1



Overflow

- For N-bit ALU

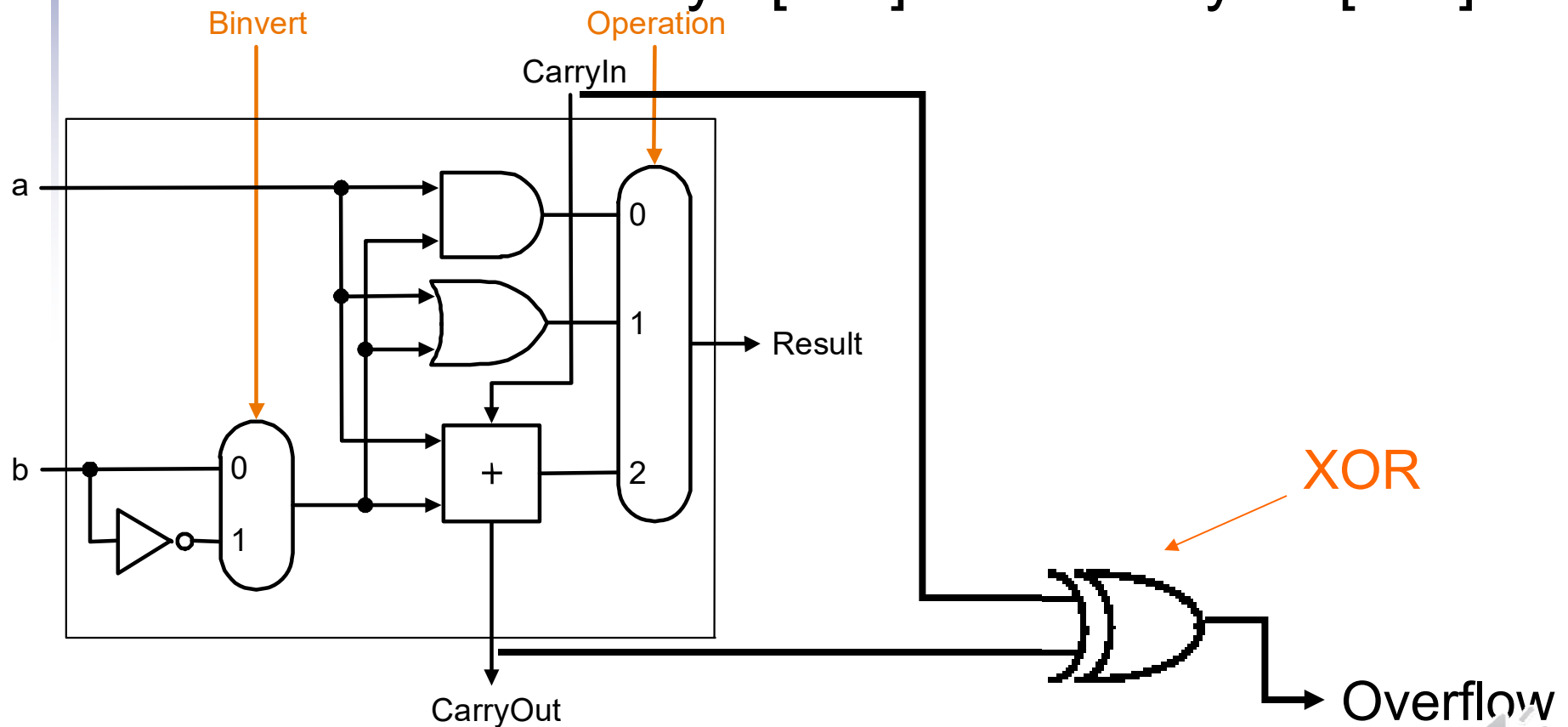- $\text{Overflow} = \text{CarryIn}[N-1] \text{ XOR } \text{CarryOut}[N-1]$



Most significant (N-1) bit ALU




Zero Detection

- Conditional Branches
- One big NOR gate
- $\text{Zero} = (\text{Result}_{N-1} + \text{Result}_{N-2} + \dots + \text{Result}_1 + \text{Result}_0)$
- Any non-zero result will cause zero detection output to be zero



NOR

 


Set-On-Less-Than (SLT)


- SLT produces a 1 if $rs < rt$, and 0 otherwise
 - all but least significant bit will be 0
 - how do we set the least significant bit?
 - can we use subtraction?
 - $rs - rt < 0$
 - set the least significant bit to the sign-bit of $(rs - rt)$
- New input: LESS
- New output: SET



SLT Implementation

 

All but MSB

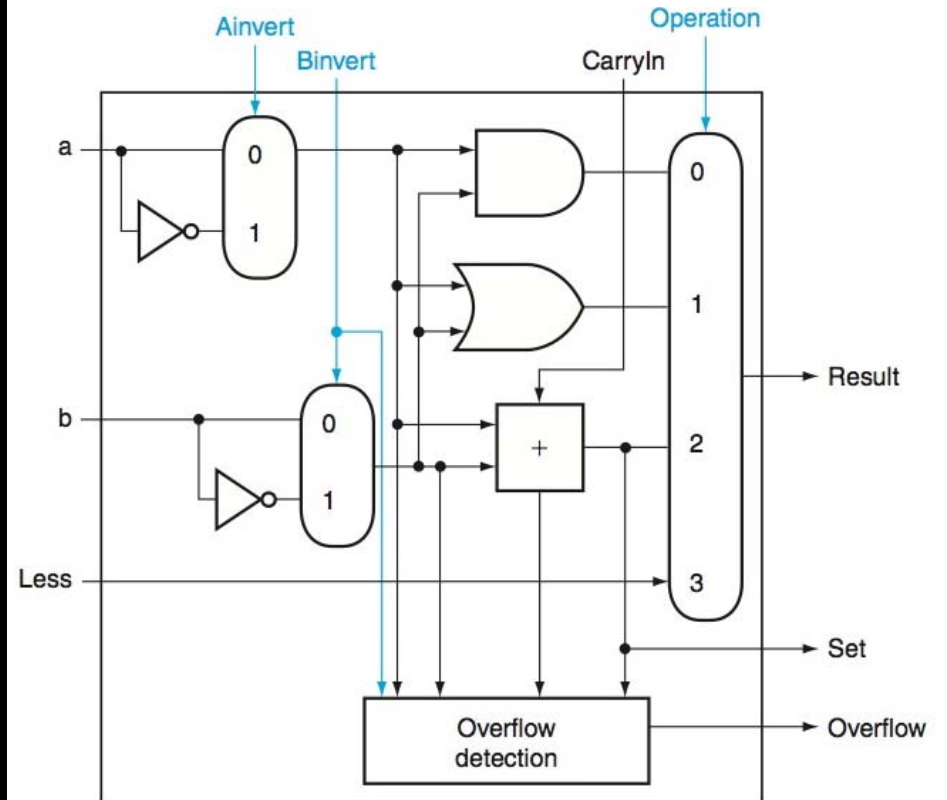


Most Significant Bit



SLT Implementation

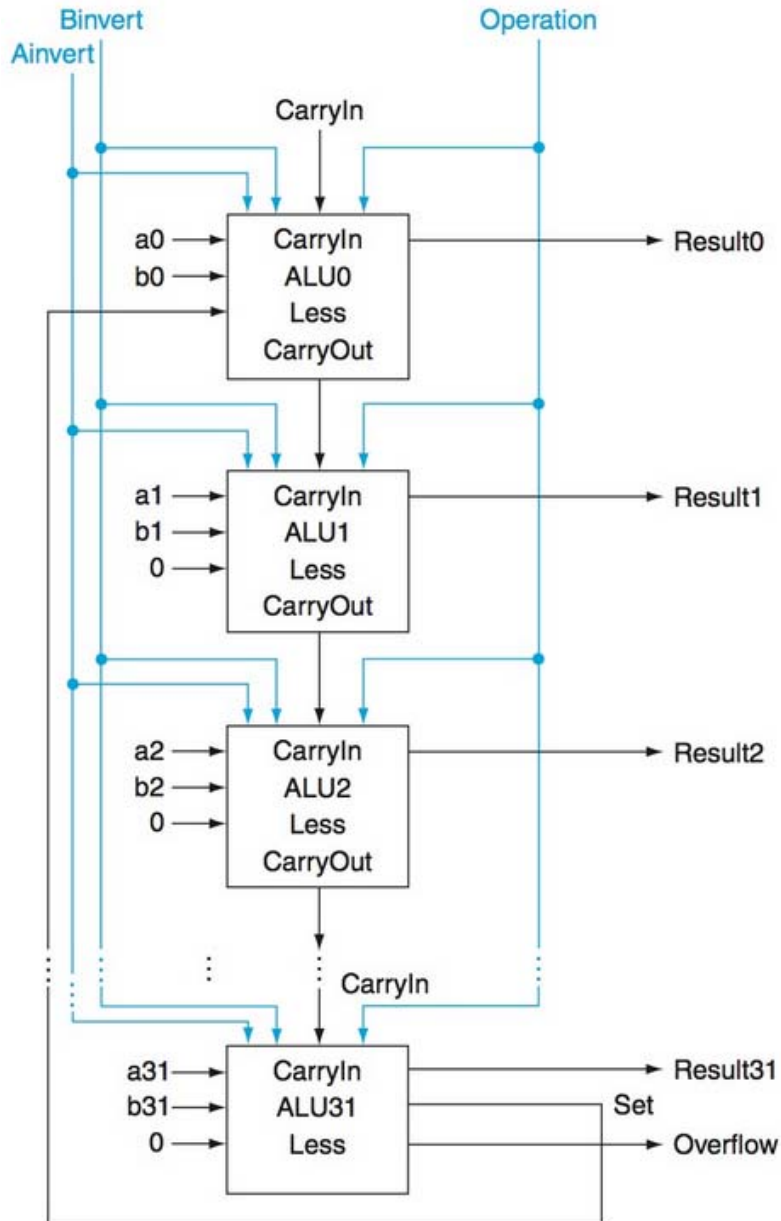- Set of MSB is connected to Less of LSB!



Final ALU

You should feel comfortable identifying what signals accomplish:

- add
- sub
- and
- or
- nor
- slt

